

# VHDL 2 – Combinational Logic Circuits

Reference: Roth/John Text: Chapter 2

# Combinational logic

---

-- Behavior can be specified as concurrent signal assignments

-- These model concurrent operation of hardware elements

entity Gates is

```
port (a, b,c: in  STD_LOGIC;  
      d:      out STD_LOGIC);
```

end Gates;

architecture behavior of Gates is

```
signal e: STD_LOGIC;
```

begin

-- concurrent signal assignment statements

```
e <= (a and b) xor (not c); -- synthesize gate-level ckt
```

```
d <= a nor b and (not e); -- in target technology
```

end;

---



# Example: SR latch (logic equations)

entity SRLatch is

```
port (S,R: in std_logic; --latch inputs
      Q,QB: out std_logic); --latch outputs
```

```
end SRLatch;
```

architecture eqns of SRLatch is

```
signal Qi,QBi: std_logic; -- internal signals
```

```
begin
```


```
QBi <= S nor Qi; -- Incorrect would be: QB <= S nor Q;
```

```
Qi <= R nor QBi; -- Incorrect would be: Q <= R nor QB;
```

```
Q <= Qi; --drive output Q with internal Qi
```

```
QB <= QBi; --drive output QB with internal QBi
```

```
end;
```

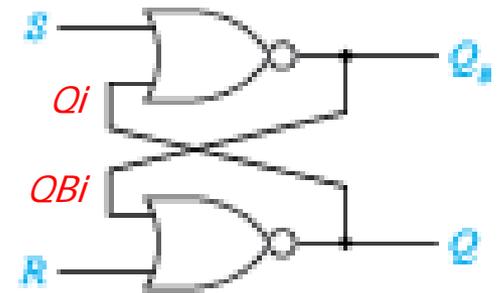

Cannot  
"reference"  
output ports.

# Conditional signal assignment (form 1)



$z \leq m$  when  $sel = '0'$  else  $n$ ;

True/False conditions

$y \leq a$  when  $(S = "00")$  else  
 $b$  when  $(S = "01")$  else  
 $c$  when  $(S = "10")$  else  
 $d$ ;

Condition can be any Boolean expression

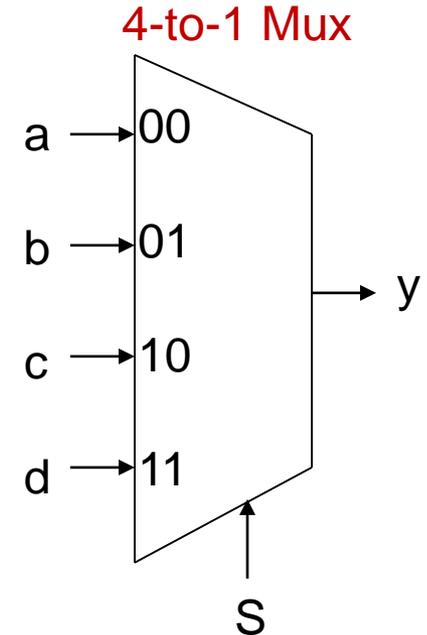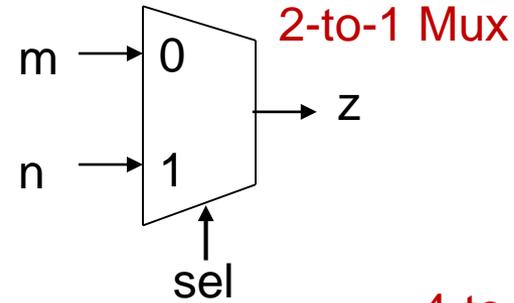$y \leq a$  when  $(F = '1')$  and  $(G = '0')$  ...



# Conditional signal assignment (form 2)

-- One signal (*S* in this case) selects the result

```
signal a,b,c,d,y: std_logic;
```

```
signal S: std_logic_vector(0 to 1);
```

```
begin
```

```
  with S select
```

```
    y <= a when "00",
```

```
        b when "01",
```


```
        c when "10",
```

```
        d when "11";
```

--Alternative "default" \*:

```
  d when others;
```

4-to-1 Mux

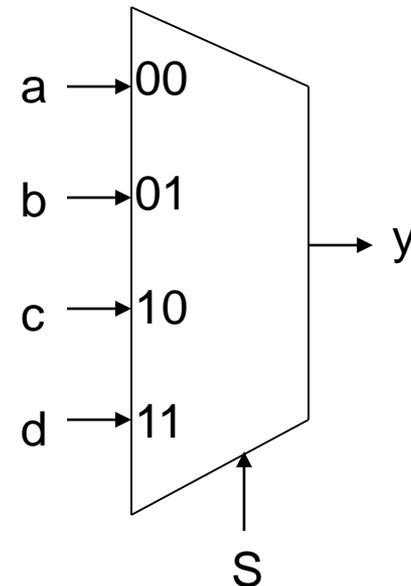

\* "std\_logic" values can be other than '0' and '1'

# 32-bit-wide 4-to-1 multiplexer

---

```
signal a,b,c,d,y: std_logic_vector(0 to 31);
```

```
signal S: std_logic_vector(0 to 1);
```

```
begin
```

```
  with S select
```


```
    y <= a when "00",
```

```
        b when "01",
```

```
        c when "10",
```

```
        d when "11";
```
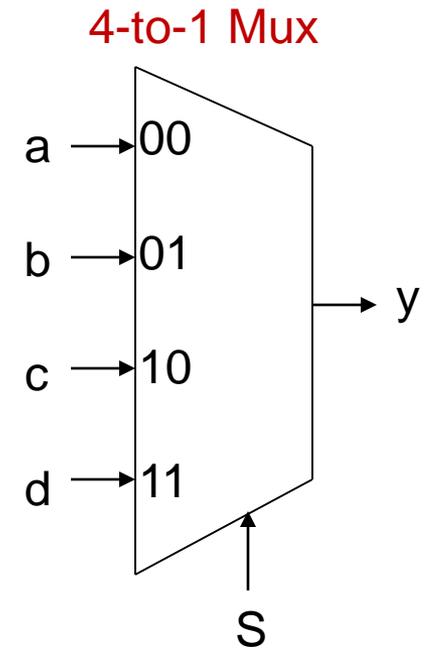
```
--y, a,b,c,d can be any type, as long as they match
```



# 32-bit-wide 4-to-1 multiplexer

-- Delays can be specified if desired

```
signal a,b,c,d,y: std_logic_vector(0 to 31);
```

```
signal S: std_logic_vector(0 to 1);
```


```
begin
```

```
with S select
```

```
y <= a after 1 ns when "00",  
     b after 2 ns when "01",  
     c after 1 ns when "10",  
     d when "11";
```

Optional non-delta  
delays for each option

4-to-1 Mux

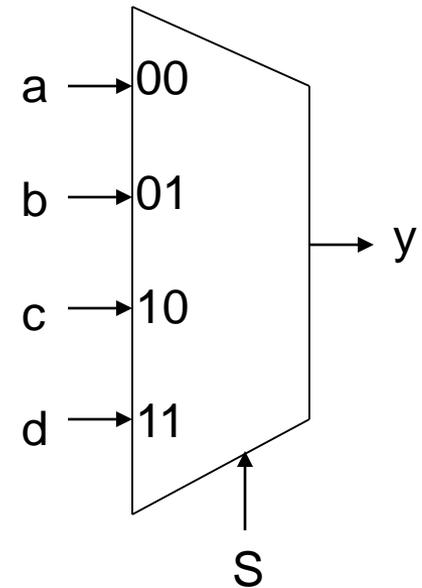

a->y delay is 1ns, b->y delay is 2ns, c->y delay is 1ns, **d->y delay is  $\delta$**

# Truth table model as a conditional assignment

- ▶ Conditional assignment can model the truth table of a switching function (without deriving logic equations)

S



A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

```
signal S: std_logic_vector(1 downto 0);
begin
  S <= A & B;      -- S(1)=A, S(0)=B
  with S select -- 4 options for S
    Y <= '0' when "00",
      '1' when "01",
      '1' when "10",
      '0' when "11",
      'X' when others;
```

& is the concatenate operator, merging scalars/vectors into larger vectors

# Example: full adder truth table

`ADDin <= A & B & Cin;` --ADDin is a 3-bit vector

`S <= ADDout(0);` --Sum output (ADDout is a 2-bit vector)

`Cout <= ADDout(1);` --Carry output

with ADDin select

`ADDout <= "00"` when "000",  
"01" when "001",  
"01" when "010",  
"10" when "011",  
"01" when "100",  
"10" when "101",  
"10" when "110",  
"11" when "111",  
"XX" when others;


ADDout			ADDin	
A	B	Cin	Cout	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


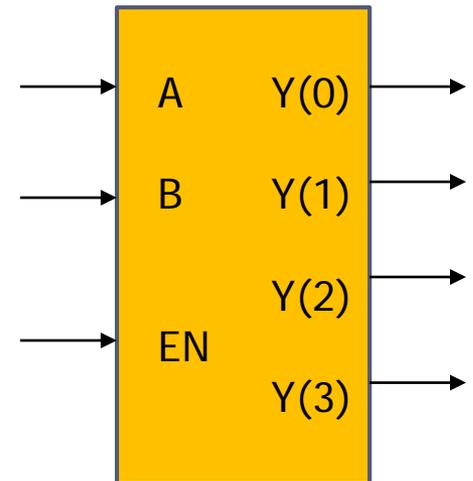
# Example: 2-to-4 decoder

---

```
library ieee; use ieee.std_logic_1164.all;
entity decode2_4 is
  port (A,B,EN: in std_logic;
        Y: out std_logic_vector(3 downto 0));
end decode2_4;
architecture behavior of decode2_4 is
  signal D: std_logic_vector(2 downto 0);
begin
  D <= EN & B & A; -- vector of the three inputs
  with D select
    Y <= "0001" when "100", --enabled, BA=00
        "0010" when "101", --enabled, BA=01
        "0100" when "110", --enabled, BA=10
        "1000" when "111", --enabled, BA=11
        "0000" when others; --disabled (EN = 0)
end;
```




# Structural model (no “behavior” specified)

---

architecture structure of full\_add1 is

```
component xor      -- declare component to be used
  port (x,y: in std_logic;
        z: out std_logic); library entity architecture
end component;
for all: xor use entity work.xor(eqns); -- if multiple arch's in lib.
signal x1: std_logic; -- signal internal to this component
begin -- instantiate components with “map” of connections
  G1: xor port map (a, b, x1);      -- instantiate 1st xor gate
  G2: xor port map (x1, cin, sum); -- instantiate 2nd xor gate
  ...add circuit for carry output...
end;
```

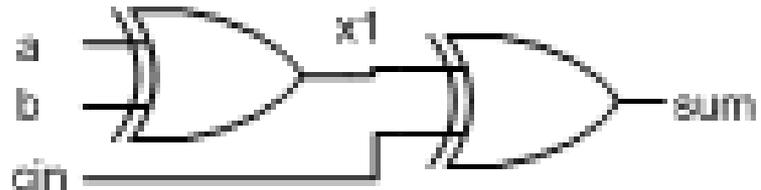

# Associating signals with formal ports

---

```
component AndGate
  port (Ain_1,Ain_2 : in std_logic; -- formal parameters
        Aout : out std_logic);
end component;
```

```
begin
```

```
-- positional association of “actual” to “formal”
```


```
A1:AndGate port map (X,Y,Z1);
```

```
-- named association (usually improves readability)
```

```
A2:AndGate port map (Ain_2=>Y, Aout=>Z2, Ain_1=>X);
```

```
-- both (positional must begin from leftmost formal)
```
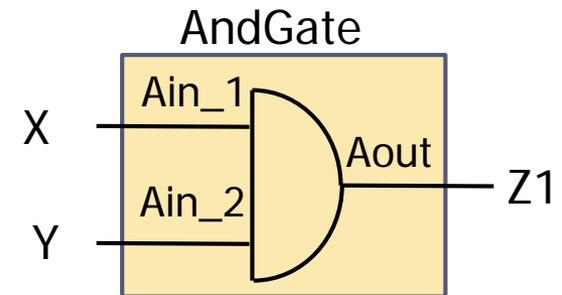
```
A3:AndGate port map (X, Aout => Z3, Ain_2 => Y);
```




# Example: D flip-flop (equations model)

---

entity DFF is

```
port (Preset: in std_logic;  
      Clear: in std_logic;  
      Clock: in std_logic;  
      Data: in std_logic;  
      Q: out std_logic;  
      Qbar: out std_logic);
```

```
end DFF;
```

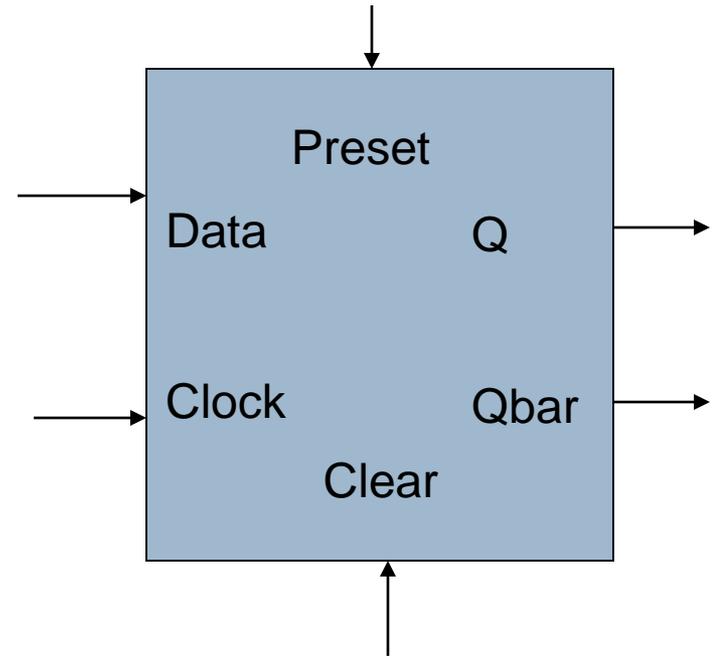

# 7474 D flip-flop equations

---

architecture eqns of DFF is

```
signal A,B,C,D: std_logic;
```

```
signal QInt, QBarInt: std_logic;
```

```
begin
```

```
A <= not (Preset and D and B) after 1 ns;
```

```
B <= not (A and Clear and Clock) after 1 ns;
```

```
C <= not (B and Clock and D) after 1 ns;
```

```
D <= not (C and Clear and Data) after 1 ns;
```

```
QInt <= not (Preset and B and QBarInt) after 1 ns;
```

```
QBarInt <= not (QInt and Clear and C) after 1 ns;
```

```
Q <= QInt;           -- Can drive but not read "outs"
```

```
QBar <= QBarInt;    -- Can read & drive "internals"
```

```
end;
```

---




# 4-bit Register (Structural Model)

---

entity Register4 is

```
port ( D: in std_logic_vector(0 to 3);  
      Q: out std_logic_vector(0 to 3);  
      Clk: in std_logic;  
      Clr: in std_logic;  
      Pre: in std_logic);
```

```
end Register4;
```

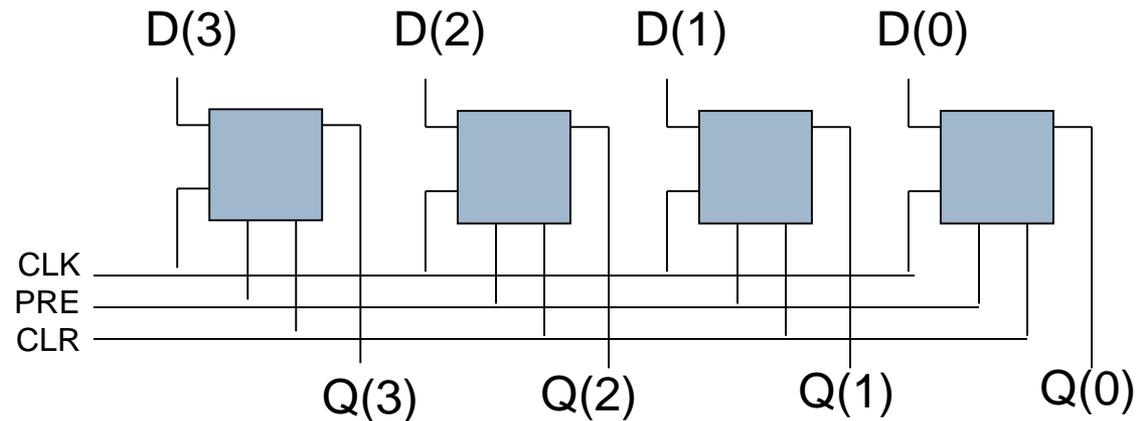

# Register Structure

---

architecture structure of Register4 is

```
component DFF    -- declare library component to be used
```

```
  port (Preset: in std_logic;  
        Clear: in std_logic;  
        Clock: in std_logic;  
        Data: in std_logic;  
        Q: out std_logic;  
        Qbar: out std_logic);
```

```
end component;
```

```
signal Qbar: std_logic_vector(0 to 3); -- dummy for unused FF Qbar outputs
```

```
begin
```

```
-- Signals connect to ports in order listed above
```

```
F3: DFF port map (Pre, Clr, Clk, D(3), Q(3), Qbar(3));
```

```
F2: DFF port map (Pre, Clr, Clk, D(2), Q(2), Qbar(2));
```

```
F1: DFF port map (Pre, Clr, Clk, D(1), Q(1), Qbar(1));
```

```
F0: DFF port map (Pre, Clr, Clk, D(0), Q(0), Qbar(0));
```

```
end;
```

---



# Register Structure (with open output)

---

architecture structure of Register4 is

```
component DFF          -- declare library component to be used
```

```
port (Preset: in std_logic;  
      Clear: in std_logic;  
      Clock: in std_logic;  
      Data: in std_logic;  
      Q: out std_logic;  
      Qbar: out std_logic);
```

```
end component;
```

```
begin
```

```
-- Signals connect to ports in order listed above
```

```
F3: DFF port map (Pre, Clr, Clk, D(3), Q(3), OPEN);
```

```
F2: DFF port map (Pre, Clr, Clk, D(2), Q(2), OPEN);
```

```
F1: DFF port map (Pre, Clr, Clk, D(1), Q(1), OPEN);
```

```
F0: DFF port map (Pre, Clr, Clk, D(0), Q(0), OPEN);
```

```
end;
```

↑ Keyword OPEN indicates  
an unconnected output



# VHDL “Process” Construct

---

(Processes will be covered in more detail in “sequential circuit modeling”)

```
[label:] process (sensitivity list)  
    declarations  
begin  
    sequential statements  
end process;
```

- ▶ Process statements are executed *in sequence*
  - ▶ Process statements are executed once at start of simulation
  - ▶ Process halts at “end” until an event occurs on a signal in the “sensitivity list”
  - ▶ Allows conventional programming language methods to describe circuit behavior
- 



# Modeling combinational logic as a process

---

-- All signals referenced in process must be in the sensitivity list.

entity And\_Good is

port (a, b: in std\_logic; c: out std\_logic);

end And\_Good;

architecture Synthesis\_Good of And\_Good is

begin

process (a,b) -- gate sensitive to events on (a, b)

begin

c <= a and b; -- c updated on a or b “events”

end process;

end;

---



# Bad example of combinational logic

---

-- This example produces unexpected results.

```
entity And_Bad is
```

```
    port (a, b: in std_logic; c: out std_logic);
```

```
end And_Bad;
```

```
architecture Synthesis_Bad of And_Bad is
```

```
begin
```

```
    process (a)          -- sensitivity list should be (a, b)
```

```
    begin
```

```
        c <= a and b; -- will not react to changes in b
```

```
    end process;
```

```
end Synthesis_Bad;
```

-- synthesis may generate a flip flop, triggered by signal a

